



ANSWER BOOK

Charging and discharging

Capacitance · Year 13

AQA 3.7.4.4 · CIE 19.3 · OCR A 6.1.3

10 questions · 30 marks

NAVY EDITION

SECTION A · Warm-up

- A1** It is an exponential decay: the charge starts at its maximum and falls, quickly at first [2]
then ever more slowly, approaching zero but never quite reaching it.
- A2** The current is greatest at the instant charging begins and decreases exponentially [2]
towards zero as the capacitor becomes fully charged.
- A3** The current equals the gradient of the charge–time graph, $I = \Delta Q / \Delta t$. [2]

SECTION B · Standard

- B1** $I_0 = V/R = 12/1000 = 0.012 \text{ A}$ (12 mA). [3]
- B2** Initial current $I_0 = V/R = 6.0/2000 = 0.0030 \text{ A}$ (3.0 mA). The final current is 0, once the [3]
capacitor is fully charged.
- B3** The pd across the capacitor rises exponentially from 0 towards the supply voltage: as [4]
charge builds up, the pd across the resistor falls, so charging slows. The current starts
at V/R and falls exponentially to zero, because the decreasing pd across the resistor
(supply minus capacitor pd) drives an ever smaller current.
- B4** $Q = CV = 100 \times 10^{-6} \times 9.0 = 9.0 \times 10^{-4} \text{ C}$. $E = \frac{1}{2}CV^2 = \frac{1}{2} \times 100 \times 10^{-6} \times 9.0^2 = 4.050 \times 10^{-3} \text{ J}$. [3]

SECTION C · Stretch

- C1** (a) $Q_0 = CV = 470 \times 10^{-6} \times 10 = 4.70 \times 10^{-3} \text{ C}$. (b) $I_0 = V/R = 10/2200 = 4.55 \times 10^{-3} \text{ A}$ (4.5 [4]
mA).
- C2** All the stored energy is dissipated: $E = \frac{1}{2}CV^2 = \frac{1}{2} \times 1000 \times 10^{-6} \times 12^2 = 0.072 \text{ J}$. [4]
- C3** As the capacitor discharges, its charge and therefore the pd across it fall. Since the [3]
current is this pd divided by the resistance ($I = V/R$), a smaller pd drives a smaller
current, so the current decreases as the discharge proceeds.