



ANSWER BOOK

EMF and internal resistance

Electricity · Year 12

AQA 3.5.1.6 · CIE 10.1 · OCR A 4.2.2, 4.3.2

10 questions · 30 marks

NAVY EDITION

SECTION A · Warm-up

- A1** The emf is the energy transferred to each unit of charge by the source, $\varepsilon = W/Q$. It is measured in volts (joules per coulomb). [2]
- A2** $V = \varepsilon - Ir = 6.0 - 0.50 \times 1.0 = 5.5 \text{ V}$. [2]
- A3** $\varepsilon = I(R + r)$, where R is the external resistance and r the internal resistance. [2]

SECTION B · Standard

- B1** $I = \varepsilon / (R + r) = 12 / (5.0 + 1.0) = 2.0 \text{ A}$. [3]
- B2** (a) $I = 9.0 / (4.0 + 0.50) = 2.0 \text{ A}$. (b) $V = IR = 2.0 \times 4.0 = 8.0 \text{ V}$. (c) $P_{\text{internal}} = I^2 r = 2.0^2 \times 0.50 = 2.0 \text{ W}$. [4]
- B3** Lost volts $= \varepsilon - V = 1.5 - 1.35 = 0.15 \text{ V}$. $r = (\varepsilon - V) / I = 0.15 / 0.30 = 0.50 \Omega$. [3]
- B4** $I = \varepsilon / r = 6.0 / 0.20 = 30 \text{ A}$. [3]

SECTION C · Stretch

- C1** From $V = \varepsilon - Ir$: the intercept is the emf, $\varepsilon = 1.5 \text{ V}$, and the gradient is $-r$, so $r = 0.5 \Omega$. At 1.0 A : $V = 1.5 - 0.5 \times 1.0 = 1.0 \text{ V}$. [4]
- C2** Lost volts $= 12 - 10 = 2.0 \text{ V}$, so $I = (\varepsilon - V) / r = 2.0 / 2.0 = 1.0 \text{ A}$. Then $R = V / I = 10 / 1.0 = 10 \Omega$. [4]
- C3** Some energy per unit charge is used driving the current through the battery's own internal resistance, giving 'lost volts' Ir . As the current increases, Ir increases, so the terminal pd $(\varepsilon - Ir)$ available to the external circuit falls. [3]