



## QUESTION WORKBOOK

# EMF and internal resistance

Electricity · Year 12

AQA 3.5.1.6 · CIE 10.1.3, 10.1.4, 10.1.5

OCR A 4.2.2(b), 4.2.2(c), 4.2.2(d), 4.3.2(a), 4.3.2(b), 4.3.2(c)(i), 4.3.2(c)(ii)

19 questions · 58 marks

NAVY SCREEN EDITION

**SECTION A** · Warm-up

**A1** Define the electromotive force (emf) of a source. [2]

---

---

---

**A2** A battery of emf 6.0 V and internal resistance  $1.0 \, \Omega$  supplies a current of 0.50 A. Calculate its terminal potential difference. [2]

**A3** State the equation linking emf, current, external resistance and internal resistance. [2]

---

---

**A4** State the condition under which the terminal pd of a cell equals its emf. [1]

---

---

**A5** A battery of emf 9.0 V has a terminal pd of 8.4 V while supplying a current. Calculate the lost volts, and state where the corresponding energy is transferred. [2]

- A6** Explain why a digital voltmeter of very high resistance connected directly across an isolated cell reads almost exactly the cell's emf. [2]

---

---

---

## SECTION B · Standard

- B1** A cell of emf 12 V and internal resistance  $1.0\ \Omega$  is connected to an external resistor of  $5.0\ \Omega$ . Calculate the current in the circuit. [3]

---

---

---

---

---

---

---

---

---

---

- B2** A battery of emf 9.0 V and internal resistance  $0.50\ \Omega$  is connected to a  $4.0\ \Omega$  resistor. Calculate (a) the current, (b) the terminal potential difference and (c) the power dissipated inside the battery. [4]

---

---

---

---

---

---

---

---

---

---

- B3** A cell of emf 1.5 V delivers a current of 0.30 A, and its terminal potential difference falls to 1.35 V. Calculate the internal resistance of the cell. [3]

---

---

---

---

---

---

---

---

---

---

- B4** A cell of emf 6.0 V has an internal resistance of 0.20  $\Omega$ . Calculate the current if its terminals are short-circuited ( $R = 0$ ). [2]

- B5** A battery has a terminal pd of 5.7 V when supplying a current of 0.60 A, and 5.1 V when supplying 1.8 A. Determine the internal resistance and the emf of the battery. [4]

- B6** A car battery of emf 12.6 V and internal resistance 25 m $\Omega$  supplies 160 A to the starter motor. Calculate the terminal pd of the battery, and determine the fraction of the battery's power that is delivered to the external circuit. [4]

- B7** A cell of emf 6.0 V and internal resistance  $0.50\ \Omega$  is connected to two  $5.0\ \Omega$  resistors in parallel. Calculate the current supplied by the cell and the cell's terminal pd. [3]

### SECTION C · Stretch

- C1** A graph of terminal potential difference  $V$  against current  $I$  for a cell is a straight line with a  $V$ -axis intercept of 1.5 V and a gradient of  $-0.5\ \text{V A}^{-1}$ . State the emf and internal resistance, and calculate the terminal pd when the current is 1.0 A. [4]

- C2** A battery of emf 12 V and internal resistance  $2.0\ \Omega$  is connected to a variable resistor. Calculate the resistance value that makes the terminal potential difference equal to 10 V. [4]

**C3** Explain why the terminal potential difference of a battery falls as it supplies a larger current. [3]

---

---

---

**C4** Describe an experiment to determine the emf and internal resistance of a cell using a variable resistor, an ammeter and a voltmeter. Explain how the results are processed, and why this method gives a better value for the emf than a single voltmeter reading across the cell. [6]

---

---

---

---

---

---

---

---

**C5** A model boat's motor needs a pd of at least 4.4 V across it while drawing 2.0 A. Two batteries are available: battery P (emf 6.0 V, internal resistance 0.90  $\Omega$ ) and battery Q (emf 5.0 V, internal resistance 0.20  $\Omega$ ). Deduce which battery should be used. [4]

- C6** Two identical cells, each of emf 1.5 V and internal resistance  $0.30\ \Omega$ , are connected in series to a  $2.4\ \Omega$  resistor. Calculate the current in the circuit and the pd across the resistor. [3]